

Oregon State University

School of EECS

ECE 499/599 – Digital VLSI Design Automation

Laboratory Design Project Report

Name: Yu-Chuan Tseng

Student ID: 934619336

1. Introduction

This project implements a 4-bit serial-input, serial-output multiplier using CMOS standard cell design flow, including:

- Verilog design
- Simulation (Xcelium/SimVision)
- Synthesis (Genus)
- Place & Route (Innovus)

The system accepts serial inputs and produces serial outputs controlled by an FSM.

2. Core Functional Blocks

2.1 4-bit x 4-bit Multiplier


Functional Description

The 4-bit $\times$ 4-bit multiplier is a purely combinational circuit that generates an 8-bit output from two 4-bit inputs A and B.

Partial products are first generated using bitwise AND operations between bits of A and B. These partial products are then summed using half-adders and full-adders arranged in a column-wise structure.

The computation is completed within a single clock cycle, and the output remains stable as long as the inputs do not change.

Block Diagram

 

Verilog Implementation& Testbench

```
tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier599—
GNU nano 5.6.1 multiplier4x4.v
wire s6, c6;

// =====
// Output bit P[0]
// =====
assign P[0] = p00;

// =====
// Column for P[1]
// P[1] = p10 + p01
// =====
ha HA1 (
    .a    (p10),
    .b    (p01),
    .sum   (P[1]),
    .carry(c1)
);

// =====
// Column for P[2]
// bits involved: p20, p11, p02, and carry from previous col
// =====
fa FA1 (
    .a    (p20),
    .b    (p11),
    .cin   (p02),
    .sum   (s2a),
    .carry(c2a)
);

ha HA2 (
    .a    (s2a),
    .b    (c1),
    .sum   (P[2]),
    .carry(c2b)
);
```

```
tsenyuch@eng
GNU nano 5.6.1
timescale 1ns/1ps

module tb_multiplier4x4;

reg  [3:0] A;
reg  [3:0] B;
wire [7:0] P;

// Instantiate the multiplier
multiplier4x4 uut (
    .A(A),
    .B(B),
    .P(P)
);

initial begin

    $display("A  B  |  P (Expected)");
    $display("-----");

    A = 4'd3; B = 4'd5; #10;
    $display("%d  %d  |  %d (15)", A, B, P);

    A = 4'd7; B = 4'd9; #10;
    $display("%d  %d  |  %d (63)", A, B, P);

    A = 4'd15; B = 4'd15; #10;
    $display("%d  %d  |  %d (225)", A, B, P);

    A = 4'd4; B = 4'd6; #10;
    $display("%d  %d  |  %d (24)", A, B, P);

    A = 4'd0; B = 4'd12; #10;
    $display("%d  %d  |  %d (0)", A, B, P);

    A = 4'd10; B = 4'd3; #10;
    $display("%d  %d  |  %d (30)", A, B, P);

    $display("-----");
    $display("Simulation finished.");

    $finish;

end

endmodule
```


Simulation Results

The 4-bit multiplier is implemented using a structural design approach. Partial products are first generated using bitwise AND operations, and the final result is obtained through column-wise accumulation.


Each output bit is computed using a combination of half-adders (HA) and full-adders (FA). For example, the least significant bit P[0] is directly assigned from the partial product p00. The next bit P[1] is computed using a half-adder that sums p10 and p01.

For higher-order bits such as P[2], multiple partial products and carry signals are combined using a full-adder followed by a half-adder, demonstrating carry propagation across columns.

 This structure ensures a purely combinational implementation and clearly exposes the critical path through cascaded adders.



Synthesis Results (Genus)

 

2.2 8-bit Serial-to-Parallel

Functional Description:

The S2P module converts serial input data into an 8-bit parallel output.

Inputs:

- clk: system clock
- reset: clears register
- shift_en: enables shifting
- in: serial input bit


Output:

- B[7:0]: parallel output

Operation:

On each rising clock edge, when shift_en is asserted, the input bit is shifted into the register. After 8 clock cycles, the full 8-bit value is available at the output.

Block Diagram

 

Verilog Implementation & Testbench

```
tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier599-
GNU nano 5.6.1 s2p_8bit.v
timescale 1ns/1ps

module s2p_8bit (
    input    clk,
    input    reset,
    input    shift_en,
    input    in,
    output [3:0] A,
    output [3:0] B
);

    reg [7:0] shift_reg;

    always @(posedge clk or posedge reset) begin
        if (reset)
            shift_reg <= 8'b00000000;
        else if (shift_en)
            shift_reg <= {shift_reg[6:0], in};
        end

    assign A = shift_reg[7:4];
    assign B = shift_reg[3:0];

endmodule
```

```
tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier599-
GNU nano 5.6.1
timescale 1ns/1ps

module tb_s2p_8bit;

    reg        clk;
    reg        reset;
    reg        shift_en;
    reg        in;
    wire [3:0] A;
    wire [3:0] B;

    s2p_8bit uut (
        .clk(clk),
        .reset(reset),
        .shift_en(shift_en),
        .in(in),
        .A(A),
        .B(B)
    );

    // 10ns clock period
    always #5 clk = ~clk;

    initial begin
        clk      = 1'b0;
        reset    = 1'b1;
        shift_en = 1'b0;
        in       = 1'b0;

        // Reset
        #12;
        reset    = 1'b0;
        shift_en = 1'b1;


        // Shift in: 1011_0101
        // Expect A = 1011, B = 0101
        in = 1'b1; #10;
        in = 1'b0; #10;
        in = 1'b1; #10;
        in = 1'b1; #10;
        in = 1'b0; #10;
        in = 1'b1; #10;
        in = 1'b0; #10;
        in = 1'b1; #10;
        in = 1'b0; #10;
        in = 1'b1; #10;

        shift_en = 1'b0;
        #10;

        $display("A = %b (expected 1011)", A);
        $display("B = %b (expected 0101)", B);

        if (A == 4'b1011 && B == 4'b0101)
            $display("PASS: S2P works correctly.");
        else
    end
```

Simulation Results

 


The Serial-to-Parallel (S2P) converter was verified using Cadence Xcelium and SimVision. During simulation, serial input data was applied sequentially while the shift enable signal was asserted.

As shown in the waveform, the input bits are shifted into the register on each clock cycle. After the required number of cycles, the parallel output matches the expected value. For example, the final output B = 0101 confirms correct operation of the S2P module.

Synthesis Results (Genus)

/stak/users/tsenyuch/ECE499/cadence/final_project/Innovus_Example_499/synthesis — eng-analogsim3.eecs.oregonstate.edu

online help **cadence**

 

2.3 8-bit Parallel-to-Serial

Functional Description:

The Parallel-to-Serial (P2S) module converts an 8-bit parallel input into a serial output stream.

Inputs:

- clk: system clock
- reset: clears the register
- load: loads parallel data

- shift_en: enables shifting

- P[7:0]: parallel input


Output:

- out: serial output

Operation:

When load is asserted, the parallel input is stored into the register. When shift_en is enabled, the data is shifted out one bit per clock cycle, starting from the most significant bit.


Block Diagram

 

Verilog Implementation & Testbench

```
tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier599.  
GNU nano 5.6.1 p2s_8bit.v  
timescale 1ns/1ps  
  
module p2s_8bit (  
    input    clk,  
    input    reset,  
    input    load,  
    input    shift_en,  
    input [7:0] data_in,  
    output   out  
);  
  
    reg [7:0] shift_reg;  
  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_reg <= 8'b0;  
        else if (load)  
            shift_reg <= data_in;  
        else if (shift_en)  
            shift_reg <= {shift_reg[6:0], 1'b0};  
        end  
  
    assign out = shift_reg[7];  
  
endmodule  
  
tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier599.  
GNU nano 5.6.1  
timescale 1ns/1ps  
  
module tb_p2s_8bit;  
  
    reg clk;  
    reg reset;  
    reg load;  
    reg shift_en;  
    reg [7:0] data_in;  
    wire out;  
  
    p2s_8bit uut (  
        .clk(clk),  
        .reset(reset),  
        .load(load),  
        .shift_en(shift_en),  
        .data_in(data_in),  
        .out(out)  
    );  
  
    always #5 clk = ~clk;  
  
    initial begin  
        clk = 0;  
        reset = 1;  
        load = 0;  
        shift_en = 0;  
        data_in = 8'b0;  
  
        #12;  
        reset = 0;  
  
        // Load data = 10110101  
        data_in = 8'b10110101;  
        load = 1;  
        #10;  
        load = 0;  
  
        // First bit should already be visible at out  
        $display("Expected serial output: 1 0 1 1 0 1 0 1");  
        $write("Actual serial output: ");  
        $write("%b ", out);  
  
        shift_en = 1;  
  
        repeat(7) begin  
            #10;  
            $write("%b ", out);  
        end  
  
        $display("");  
        #10;  
        $finish;  
    end  
end
```

Simulation Results

 


The Parallel-to-Serial (P2S) converter was verified using Cadence Xcelium and SimVision. A parallel input value was first loaded into the register when the load signal was asserted.

After loading, the shift enable signal was activated, and the data was shifted out serially on each clock cycle. The waveform shows that the output bits are produced sequentially and match the expected serial output.

For example, for an input value of 0xB5, the output sequence is 1 0 1 1 0 1 0 1, which matches the expected result, confirming correct operation of the P2S module.

Synthesis Results (Genus)

 

2.4 Controller FSM

Functional Description:

The controller is implemented as a Moore finite state machine (FSM) that manages the operation of the system.

Inputs:

- clk, reset, start

Outputs:

- s2p_shift_en

- p2s_load

- p2s_shift_en


- done

Operation:

The FSM controls the sequence of operations, including loading input data, triggering the multiplier, and shifting out the result.

The system starts in the IDLE state. When start is asserted, the FSM enables input shifting (LOAD_IN), then loads the result into the output register (LOAD_P2S), and finally shifts out the result (SHIFT_OUT). The done signal is asserted at the end of the operation.

Block Diagram

 

Verilog Implementation & Testbench

```
tsenyuch@eng-analogsim3:~/ECE499/cadence/fina
GNU nano 5.6.1      contr
`timescale 1ns/1ps

module controller_fsm(

    input clk,
    input reset,
    input start,

    output reg s2p_shift_en,
    output reg p2s_load,
    output reg p2s_shift_en,
    output reg done
);

    // FSM states
    localparam IDLE      = 3'd0;
    localparam LOAD_IN   = 3'd1;
    localparam LOAD_P2S  = 3'd2;
    localparam SHIFT_OUT = 3'd3;
    localparam DONE_ST  = 3'd4;

    reg [2:0] state, next_state;
    reg [3:0] counter;

    //-----
    // State register
    //-----
    always @(posedge clk or posedge reset) begin
        if (reset)
            state <= IDLE;
        else
            state <= next_state;
    end
```

The Verilog implementation of the controller FSM is divided into three parts: the state register, the next-state logic, and the output logic. The state register is updated on the rising edge of the clock or reset, the next-state logic is implemented using a combinational case statement, and the control outputs are generated according to the active state. This structure improves readability and clearly separates sequential and combinational behavior.

```
GNU nano 5.6.1
`timescale 1ns/1ps

module tb_controller_fsm;

    reg clk;
    reg reset;
    reg start;

    wire s2p_shift_en;
    wire p2s_load;
    wire p2s_shift_en;
    wire done;

    controller_fsm uut(
        .clk(clk),
        .reset(reset),
        .start(start),
        .s2p_shift_en(s2p_shift_en),
        .p2s_load(p2s_load),
        .p2s_shift_en(p2s_shift_en),
        .done(done)
    );

    // clock
    always #5 clk = ~clk;

    initial begin

        clk = 0;
        reset = 1;
        start = 0;

        #12
        reset = 0;

        // start signal
        #10
        start = 1;

        #10
        start = 0;


        // let FSM run
        #200

        $finish;

    end

endmodule
```

Simulation Results

 


The controller FSM was verified using Cadence Xcelium and SimVision. The waveform demonstrates correct sequencing of control signals in response to the start signal.

Initially, the FSM remains in the IDLE state until the start signal is asserted. Upon receiving the start signal, the FSM enables the serial-to-parallel shift operation through s2p_shift_en. After the input data is fully loaded, the FSM transitions to the next stage, where p2s_load is asserted to load the parallel data into the output register.

Subsequently, the FSM enables p2s_shift_en to shift the data out serially. Finally, the done signal is asserted to indicate completion of the operation before returning to the IDLE state.

The waveform confirms that all control signals are activated in the correct order, demonstrating proper FSM operation.

Synthesis Results (Genus)

 

3. Top-Level Implementation


3.1 System Overview

The top-level system integrates the S2P module, 4x4 multiplier, P2S module, and FSM controller.


Serial input data is first converted into parallel form using the S2P block. The multiplier computes the result, which is then stored and shifted out serially using the P2S block.



The FSM coordinates all operations by generating control signals to ensure correct sequencing of input loading, computation, and output shifting.

3.2 Block Diagram

 

3.3 Timing Diagram

 

  

3.4 Verilog Implementation & Testbench

```
tsenyu
GNU nano 5.6.1
input clk,
input reset,
input start,
input in,
output out,
output done
);

// datapath wires
wire [3:0] A;
wire [3:0] B;
wire [7:0] S;

// control wires
wire s2p_shift_en;
wire p2s_load;
wire p2s_shift_en;

// Serial ? Parallel
s2p_8bit u_s2p (
    .clk(clk),
    .reset(reset),
    .shift_en(s2p_shift_en),
    .in(in),
    .A(A),
    .B(B)
);

// 4x4 multiplier
multiplier4x4 u_mult (
    .A(A),
    .B(B),
    .P(S)
);

// Parallel ? Serial
p2s_8bit u_p2s (
    .clk(clk),
    .reset(reset),
    .load(p2s_load),
    .shift_en(p2s_shift_en),
    .data_in(S),
    .out(out)
);

// Controller FSM
controller_fsm u_fsm (
    .clk(clk),
    .reset(reset),
    .start(start),
    .s2p_shift_en(s2p_shift_en),
    .p2s_load(p2s_load),
    .p2s_shift_en(p2s_shift_en),
    .done(done)
);
```

```
tsenyuch@eng-ar
GNU nano 5.6.1
timescale 1ns/1ps

module tb_serial_multiplier_top;

    reg clk;
    reg reset;
    reg start;
    reg in;

    wire out;
    wire done;

    reg [7:0] out_capture;
    integer i;

    serial_multiplier_top uut (
        .clk(clk),
        .reset(reset),
        .start(start),
        .in(in),
        .out(out),
        .done(done)
    );

    // 10ns clock period
    always #5 clk = ~clk;

    initial begin
        clk = 0;
        reset = 1;
        start = 0;
        in = 0;
        out_capture = 8'b0;

        // Reset
        #12;
        reset = 0;

        // Start pulse
        #8;
        start = 1;
        #10;
        start = 0;

        // Send serial input: A=0011, B=0101
        // Order: A3 A2 A1 A0 B3 B2 B1 B0
        in = 0; #10; // A3
        in = 0; #10; // A2
        in = 1; #10; // A1
        in = 1; #10; // A0
        in = 0; #10; // B3
        in = 1; #10; // B2
        in = 0; #10; // B1
        in = 1; #10; // B0
    end
endmodule
```




```
// Send serial input: A=0011, B=0101
// Order: A3 A2 A1 A0 B3 B2 B1 B0
in = 0; #10; // A3
in = 0; #10; // A2
in = 1; #10; // A1
in = 1; #10; // A0
in = 0; #10; // B3
in = 1; #10; // B2
in = 0; #10; // B1
in = 1; #10; // B0

// Wait until output phase begins and capture 8 serial output bits
wait(done == 1'b1);

// For current FSM, done comes after shifting out.
// So capture output during the shift-out interval by timing:
// restart sim structure could be improved later, but here we simply
// monitor expected window before done.

// This display is for debug
$display("done asserted at time %0t", $time);

#20;
$finish;
end

// Capture outgoing serial bits during shift_out window
// Since output is MSB-first, shift bits into out_capture from left to right
initial begin
    wait(reset == 0);
    wait(start == 1);

    // Wait through:
    // 8 input clocks + 1 load clock
    #(10*9);


    // Capture 8 output bits
    for (i = 0; i < 8; i = i + 1) begin
        #10;
        out_capture[7-i] = out;
    end

    #1;
    $display("Captured output = %b", out_capture);
    $display("Expected output = 00001111");


    if (out_capture == 8'b00001111)
        $display("PASS: Top-level serial multiplier works correctly.");
    else
        $display("FAIL: Top-level output mismatch.");
end

endmodule
```

3.5 Simulation Results

 

3.6 Synthesis Result

 

Timing report

tsenyuch@eng-analogsim3:~/ECE499/cadence/final_project/Multiplier59

```
=====
Generated by:      Genus(TM) Synthesis Solution 25.12-s067_1
Generated on:      Mar 18 2026 10:28:44 pm
Module:           serial_multiplier_top
Operating conditions: ss_1.62_125
Interconnect mode: global
Area mode:        physical library
=====
```

Path 1: MET (4730 ps) Late External Delay Assertion at pin done

Group: clk

Startpoint: (R) u_fsm/state_reg[1]/CK

Clock: (R) clk

Endpoint: (F) done

Clock: (R) clk

	Capture	Launch
Clock Edge:+	10000	0
Src Latency:+	0	0
Net Latency:+	0 (I)	0 (I)
Arrival:=	10000	0
Output Delay:-	4000	
Uncertainty:-	150	
Required Time:=	5850	
Launch Clock:-	0	
Data Path:-	1120	
Slack:=	4730	

Exceptions/Constraints:

output_delay	4000	constraints_top.sdc_line_11
--------------	------	-----------------------------

```
#-----
# Timing Point      Flags  Arc  Edge  Cell      Fanout Load Trans Delay Arrival Instance
#                  (fF) (ps) (ps) (ps) (ps) Location
#-----
u_fsm/state_reg[1]/CK -      -    R    (arrival) 23      -    200    0      0      (-,-)
u_fsm/state_reg[1]/Q  -      CK->Q R    SDFFRX1  5 22.8  264    750    750    (-,-)
u_fsm/g592__6783/Y    -      B->Y F    NOR2X1  2 8.3   104    166    916    (-,-)
u_fsm/g587__6260/Y    -      B->Y F    CLKAND2X2 1 1.8   34     204    1120   (-,-)
done                  <<<  -    F    (port)   -      -      -      0      1120   (-,-)
#-----
```

tsenyuch@eng-analogsim3:~/ECE499/cadence/f

Instance: /serial_multiplier_top

Power Unit: W

PDB Frames: /stim#0/frame#0

Category	Leakage	Internal	Switching	Total	Row%
memory	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.00%
register	1.87263e-07	6.34328e-05	8.37090e-06	7.19910e-05	59.36%
latch	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.00%
logic	6.76895e-08	1.86768e-05	1.96824e-05	3.84269e-05	31.68%
bbox	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.00%
clock	0.000000e+00	0.000000e+00	1.08650e-05	1.08650e-05	8.96%
pad	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.00%
pm	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.00%
Subtotal	2.54952e-07	8.21096e-05	3.89183e-05	1.21283e-04	100.00%
Percentage	0.21%	67.70%	32.09%	100.00%	100.00%

Metric	Value
Max Delay	1.12 ns
Leakage Power	0.255 μ W
Switching Power	38.9 μ W
Total Power	121.3 μ W

3.7 Maximum Clock Frequency

Worst-Case Delay Path and Maximum Clock Frequency


The post-synthesis timing report for the top-level design shows a worst-case path from u_fsm/state_reg[1]/CK to the output pin done. The reported data path delay for this path is 1120 ps, which corresponds to 1.12 ns. This value is taken as the critical path delay of the top-level system.

The maximum clock frequency is estimated from the critical path delay as:

$$f_{max} = \frac{1}{T_{critical}} = \frac{1}{1.12 \text{ ns}} \approx 892.9 \text{ MHz}$$

Therefore, the estimated maximum clock frequency of the top-level design is approximately 893 MHz.

3.8 Place and Route (Innovus)

 

Layout




Net



Snap



A

 

All Colors

Favorite

Violation

Instance

- Type
 - Block
 - StdCell
 - Cover
 - Physical
 - IO
 - Area IO
 - SpareCell
 - Black Box
- Function
- Status

Module

- Cell
- Blockage
- Row
- Floorplan
- Partition
- Power
- Overlay
- Track
- Net
- Route

Layer

- poly
- mcon(0)
- met1(1)
- via
- met2(2)
- via2(2)
- met3(3)
- via3(3)

Adaptive

Detail

Speed

select Instance Enter Instance name.

Append

coords

0, 0

radius

150

Goto

9.09600, 1.24900 Sel: 0 Routed


```

Reset AXI Options
*** time_design #2 [finish] () : cpu/real = 0:00:00.6/0:00:00.9 (0.6), totSession cpu/real = 0:00:00.6/0:00:00.9 (0.6)
@innovus 102> set_db check_drc_disable_rules {} ; set_db check_drc_check_only default ; set_db check_drc_reverse false ; set_db check_drc_short_only false ; set_db check_drc_check_routing_halo false ; set_db check_drc_trim_length false ; set_db check_drc_uncolored false ; set_db check_drc_enable_post_passes false ; set_db check_drc_ignore_non_rectangle_shapes false ; set_db check_drc_inside_via_def true ; set_db check_drc_report_outside false ; set_db check_drc_ignore_cell_blockage false ; set_db check_drc_report {} ; set_db check_drc_report_outside false
@innovus 103> check_drc
#-check_same_via_cell true          # bool, default=false, user setting
#-report                             # string, default="", user setting
*** Starting Verify DRC (MEM: 3310.9) ***

VERIFY DRC ..... Starting Verification
VERIFY DRC ..... Initializing
**WARN: (IMPVFG-1076): Unable to create a report file. verify_drc report will not be generated.
VERIFY DRC ..... Deleting Existing Violations
VERIFY DRC ..... Creating Sub-Areas
VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.000 0.000 75.440 68.080} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 4 Viols.

Verification Complete : 4 Viols.

Violation Summary By Layer and Type:

          Short  Totals
met2             4      4
Totals           4      4

*** End Verify DRC (CPU TIME: 0:00:00.0  ELAPSED TIME: 0:00:01.0  MEM: 10.6M) ***

@innovus 104> set_db check_drc_area {0 0 0 0}
@innovus 105>

```

```

@innovus 104> set_db check_drc_area {0 0 0 0}
@innovus 105>
@innovus 105> check_connectivity -type all -geometry_connect -error 1000 -warning 50
VERIFY_CONNECTIVITY use new engine.

***** Start: VERIFY CONNECTIVITY *****
Start Time: Mon Mar  9 21:26:10 2026

Design Name: serial_multiplier_top
Database Units: 1000
Design Boundary: (0.0000, 0.0000) (75.4400, 68.0800)
Error Limit = 1000; Warning Limit = 50
Check all nets

Begin Summary
  Found no problems or warnings.
End Summary

End Time: Mon Mar  9 21:26:10 2026
Time Elapsed: 0:00:00.0

***** End: VERIFY CONNECTIVITY *****
Verification Complete : 0 Viols.  0 Wrngs.
(CPU Time: 0:00:00.0  MEM: 0.062M)

```


4. Additional 599 Requirements

4.1 8-bit Multiplier Design

The 8-bit multiplier is implemented using a sequential architecture that reuses the existing 4×4 combinational multiplier to reduce hardware cost.


Instead of computing the full 8×8 multiplication in a single cycle, the operands are divided into 4-bit segments. The multiplication is performed over multiple cycles by generating partial products using the 4×4 multiplier and accumulating them with appropriate bit shifting.

At each step, a selected 4-bit portion of the operands is fed into the multiplier, and the resulting partial product is shifted according to its significance and added to an accumulator register. This process is repeated until all partial products have been generated and accumulated.

A finite state machine (FSM) controls the sequencing of operations, including input loading, partial-product generation, accumulation, and output shifting.

This approach significantly reduces area compared to a fully combinational 8×8 multiplier, at the cost of increased latency due to multi-cycle operation.

4.2 Block Diagram

 

tsenyuch@eng-analogsim3:

GNU nano 5.6.1

```

timescale 1ns/1ps

module serial_multiplier8x8_top (
    input clk,
    input reset,
    input start,
    input in,
    output out,
    output done
);

// -----
// Internal datapath wires
// -----
wire [7:0] A;
wire [7:0] B;

wire [3:0] mult_a;
wire [3:0] mult_b;
wire [7:0] mult_out;

wire [15:0] acc_out;

// -----
// Internal control wires
// -----
wire      s2p_shift_en;
wire      clear_acc;
wire      load_acc;
wire      p2s_load;
wire      p2s_shift_en;
wire [1:0] shift_sel;
wire      a_sel;
wire      b_sel;

// -----
// Serial-to-Parallel 16-bit
// -----
s2p_16bit u_s2p (
    .clk(clk),
    .reset(reset),
    .shift_en(s2p_shift_en),
    .in(in),
    .A(A),
    .B(B)
);

// -----
// Nibble select
// a_sel = 0 -> A_lo, 1 -> A_hi
// b_sel = 0 -> B_lo, 1 -> B_hi
// -----
assign mult_a = (a_sel == 1'b0) ? A[3:0] : A[7:4];
assign mult_b = (b_sel == 1'b0) ? B[3:0] : B[7:4];
endmodule

```

tsenyuch@eng-analogsim3:

GNU nano 5.6.1

```

// -----
// 4x4 multiplier
// -----
multiplier4x4 u_mult (
    .A(mult_a),
    .B(mult_b),
    .P(mult_out)
);

// -----
// Accumulate unit
// -----
accumulate_unit u_acc (
    .clk(clk),
    .reset(reset),
    .clear_acc(clear_acc),
    .load_acc(load_acc),
    .mult_out(mult_out),
    .shift_sel(shift_sel),
    .acc_out(acc_out)
);

// -----
// Parallel-to-Serial 16-bit
// -----
p2s_16bit u_p2s (
    .clk(clk),
    .reset(reset),
    .load(p2s_load),
    .shift_en(p2s_shift_en),
    .data_in(acc_out),
    .out(out)
);

// -----
// FSM controller
// -----
controller_fsm_599 u_fsm (
    .clk(clk),
    .reset(reset),
    .start(start),
    .s2p_shift_en(s2p_shift_en),
    .clear_acc(clear_acc),
    .load_acc(load_acc),
    .p2s_load(p2s_load),
    .p2s_shift_en(p2s_shift_en),
    .done(done),
    .shift_sel(shift_sel),
    .a_sel(a_sel),
    .b_sel(b_sel)
);
endmodule

```

4.3 Verilog Implementation

The `serial_multiplier8x8_top` module serves as the structural integration layer of the entire 8×8 serial multiplier. It connects the input/output conversion blocks, the reused 4×4 multiplier, the accumulation unit, and the FSM controller. The FSM determines which 4-bit portions of the operands are sent into the multiplier, how much each partial product should be shifted, and when the accumulated result should be loaded and shifted out. In this way, the top-level module coordinates all submodules into a complete

sequential multiplier system.

```
tsenyuch@eng-analogsim3
GNU nano 5.6.1
`timescale 1ns/1ps

module tb_serial_multiplier8x8;

    reg clk;
    reg reset;
    reg start;
    reg in;

    wire out;
    wire done;

    reg [15:0] out_capture;
    integer i;

    serial_multiplier8x8_top uut (
        .clk(clk),
        .reset(reset),
        .start(start),
        .in(in),
        .out(out),
        .done(done)
    );

    // 10 ns clock period
    always #5 clk = ~clk;

    // Drive reset, start, and serial input
    initial begin
        clk = 1'b0;
        reset = 1'b1;
        start = 1'b0;
        in = 1'b0;
        out_capture = 16'b0;

        // Reset
        #12;
        reset = 1'b0;

        // Start pulse
        #8;
        start = 1'b1;
        #10;
        start = 1'b0;

        // Send A = 00001101 (13), MSB first
        in = 1'b0; #10; // A7
        in = 1'b0; #10; // A6
        in = 1'b0; #10; // A5
        in = 1'b0; #10; // A4
        in = 1'b1; #10; // A3
        in = 1'b1; #10; // A2
        in = 1'b0; #10; // A1
        in = 1'b1; #10; // A0

        // Send B = 00001001 (9), MSB first
        in = 1'b0; #10; // B7
        in = 1'b0; #10; // B6
        in = 1'b0; #10; // B5
        in = 1'b0; #10; // B4
        in = 1'b1; #10; // B3
        in = 1'b0; #10; // B2
        in = 1'b0; #10; // B1
        in = 1'b1; #10; // B0

    end

    // Capture serial output when SHIFT_OUT begins
    initial begin
        out_capture = 16'b0;

        wait(reset == 1'b0);
        wait(start == 1'b1);

        // Wait until the FSM enters the output shifting phase
        wait(uut.p2s_shift_en == 1'b1);

        // Small delay to allow out to settle
        #1;

        $display("Expected output = 000000001110101");
        $write("Captured output = ");

        // Capture first output bit immediately
        out_capture[15] = out;
        $write("%b", out);

        // Capture remaining 15 bits on subsequent clock cycles
        for (i = 1; i < 16; i = i + 1) begin
            @(posedge clk);
            #1;
            out_capture[15-i] = out;
            $write("%b", out);
        end

        $display("");


        #1;
        if (out_capture == 16'b000000001110101)
            $display("PASS: serial_multiplier8x8_top works correctly.");
        else begin
            $display("FAIL: output mismatch.");
            $display("Captured = %b", out_capture);
            $display("Expected = 000000001110101");
        end

        wait(done == 1'b1);
        $display("done asserted at time %0t", $time);

        #10;
    end
endmodule
```


The testbench verifies the serial multiplier by applying serial input data and capturing the output bit-by-bit. Instead of using a fixed delay, it waits for the `p2s_shift_en` signal to ensure proper timing alignment before capturing output data. The captured result is compared with the expected value, and a PASS/FAIL message is generated automatically.

4.4 Simulation Results

 

The waveform shows the complete operation of the serial multiplier, including input loading, computation, and output shifting. The operands are serially loaded via the `in` signal, and the result is shifted out through `out`. The captured output progresses to the final value 0x0075, which matches the expected result of 13×9 . The `done` signal indicates completion of the operation.

4.5 Synthesis Results

 

The synthesized 8×8 serial multiplier meets the timing requirement under a 10 ns clock constraint with a positive slack of 0.049 ns, indicating that the design satisfies timing with a near-critical path delay. Based on this slack, the maximum path delay is approximately 9.951 ns, which corresponds to a maximum operating frequency of about 100.5 MHz.

The total cell area of the design is 10,938.7 μm^2 . Among all modules, the accumulate unit contributes the largest portion of the area, followed by the FSM controller and the parallel-to-serial (P2S) block.

The total power consumption is approximately 0.384 mW. The majority of the power is dominated by internal (62.87%) and switching (36.95%) components, while leakage power is negligible.

The execution time of the multiplier is determined by the FSM operation. The design requires 16 cycles to load inputs, 1 cycle to clear the accumulator, 4 cycles for partial-product computation, 1 cycle to load the output register, and 16 cycles to shift out the result, resulting in a total of 38 clock cycles. Therefore, the total latency is approximately 380 ns under a 10 ns clock period. If the DONE state is included, the total latency becomes 390 ns.

5. Discussion

- **How does each block work? Describe operation in terms of inputs, output, and states (where appropriate).**

The design is composed of several main functional blocks: a serial-to-parallel (S2P) input register, a finite state machine (FSM) controller, a multiplier datapath, an accumulator, and a parallel-to-serial (P2S) output register.

The S2P block receives serial input bits and converts them into parallel operands. The FSM controller governs the overall operation of the system, including loading inputs, clearing registers, enabling multiplication steps, and shifting out results. The multiplier datapath generates partial products based on the input operands, while the accumulator stores and updates intermediate results across multiple cycles. Finally, the P2S block converts the parallel multiplication result into a serial output stream.

The FSM transitions through multiple states including input loading, computation, and output shifting, ensuring correct sequencing of operations and synchronization between all blocks.

- **How did you test your design and ensure that it functions correctly with different operands and operations?**

The design was verified using a SystemVerilog testbench in Xcelium. Multiple test cases were applied to ensure correctness, including different combinations of input operands such as small values, large values, and edge cases (e.g., 0, maximum values).

Waveform analysis was performed using SimVision to confirm correct timing behavior and functional correctness. Key signals such as input loading, state transitions, accumulator updates, and output shifting were carefully examined. The output results were compared against expected multiplication values to ensure accuracy.

Additionally, corner cases such as reset behavior and sequential input loading were verified to confirm robust operation of the design.

- **What were the primary challenges that you encountered while working on the project?**

One of the primary challenges in this project was coordinating the timing between different modules, especially ensuring correct synchronization between the FSM controller and datapath operations. Managing multi-cycle operations, such as serial input loading and output shifting, required careful design of state transitions and counters.

Another challenge was debugging incorrect intermediate results due to timing or control signal issues. This required extensive waveform analysis to trace signal propagation and identify logic errors.

Additionally, understanding the synthesis results and interpreting timing and power reports from Genus required careful analysis to ensure that the design met performance constraints.

- **Is there anything you would implement differently if you were to redesign this project?**

If the design were to be improved, one potential enhancement would be to increase performance by adopting a parallel multiplier architecture instead of a serial implementation. This would significantly reduce the number of clock cycles required for computation at the cost of increased area.

Another improvement would be optimizing the FSM and datapath to reduce unnecessary states or transitions, thereby improving efficiency. Power optimization techniques, such as clock gating, could also be applied to reduce switching activity.

Finally, further optimization of the synthesis constraints and exploration of different effort levels could improve timing and area trade-offs.